


**HIGHER SECONDARY
SECOND YEAR**

PHYSICS

UNIT - 10

**ELECTRONICS
AND
COMMUNICATIONS**

PROBLEMS AND SOLUTIONS

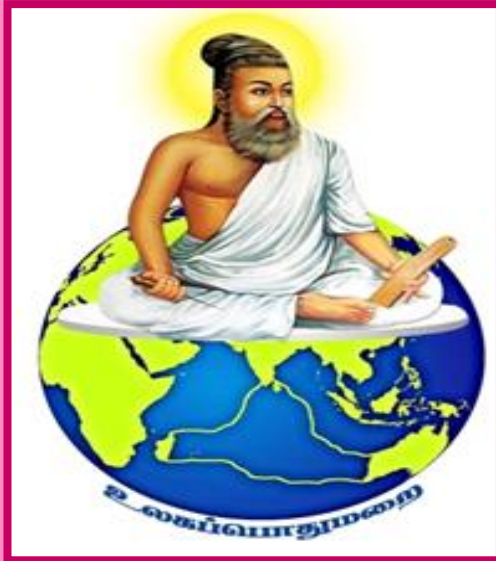

victory


R. SARAVANAN. M.Sc, M.Phil, B.Ed

PG ASST (PHYSICS)

GBHSS, PARANGIPETTAI - 608 502

EXAMPLE PROBLEMS

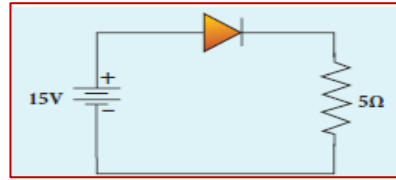1. An ideal diode and a 5Ω resistor are connected in series with a 15 V power supply as shown in figure below. Calculate the current that flows through the diode.



Solution :

- The diode is forward biased and it is an ideal one. Hence, it acts like a closed switch with no barrier voltage. Therefore, current that flows through the diode can be calculated using Ohm's law.

$$V = IR$$

$$(or) \quad I = \frac{V}{R} = \frac{15}{5} = 3 \text{ A}$$

2. A silicon diode is connected with $1 \text{ k}\Omega$ resistor as shown. Find the value of current flowing through AB .



Solution : $R = 1 \text{ k}\Omega = 1000 \Omega$

- The barrier voltage for silicon diode ; $V_b (Si) = 0.7 \text{ V}$
- The P.D. between A and B is given by ;
 $V = [V_A - V_B] - V_b (Si) = [3.3 - (-7.4)] - 0.7 = 10.7 - 0.7 = 10 \text{ V}$
- The value of current flowing through AB can be obtained using Ohm's law.

$$V = IR$$

$$(or) \quad I = \frac{V}{R} = \frac{10}{1000} = 10^{-2} \text{ A} = 10 \text{ mA}$$

3. Find the current through the Zener diode when the load resistance is $2 \text{ k}\Omega$. Use diode approximation.

Solution : $V = 15 \text{ V}$; $R_S = 1 \text{ k}\Omega = 1000 \Omega$
 $V_Z = 9 \text{ V}$; $R_L = 2 \text{ k}\Omega = 2000 \Omega$

- From figure, $V_R = V - V_Z = 15 - 9 = 6 \text{ V}$
- From Ohm's law, current through ' R_S '

$$I = \frac{V_R}{R_S} = \frac{6}{1000} = 6 \times 10^{-3} \text{ A} = 6 \text{ mA}$$

- And current through load resistance R_L


$$I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \frac{9}{2000} = 4.5 \times 10^{-3} \text{ A} = 4.5 \text{ mA}$$

- If I_Z be the current through Zener diode, then using Kirchoff's current law at junction A gives,

$$I = I_L + I_Z$$

$$(or) \quad I_Z = I - I_L = 6 - 4.5$$

$$I_Z = 1.5 \text{ mA}$$

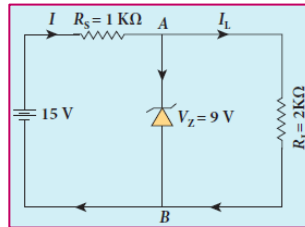

4. Determine the wavelength of light emitted from LED which is made up of GaAsP semiconductor whose forbidden energy gap is 1.875 eV . Mention the colour of the light emitted (Take $h = 6.6 \times 10^{-34} \text{ Js}$).

Solution : $E_g = 1.875 \text{ eV} = 1.875 \times 1.6 \times 10^{-19} \text{ J}$; $h = 6.6 \times 10^{-34} \text{ Js}$

- By definition,

$$E_g = h\nu = \frac{hc}{\lambda}$$

$$\therefore \lambda = \frac{hc}{E_g} = \frac{6.6 \times 10^{-34} \times 3 \times 10^8}{1.875 \times 1.6 \times 10^{-19}} = \frac{19.8 \times 10^{-7}}{3}$$

$$\lambda = 6.6 \times 10^{-7} \text{ m} = 660 \times 10^{-9} \text{ m} = 660 \text{ nm}$$

- The wavelength 660 nm corresponds to red colour light.

5. In a transistor connected in the common base configuration $\alpha = 0.95$, $I_E = 1 \text{ mA}$. Calculate the values of I_C and I_B .

Solution : $\alpha = 0.95$, $I_E = 1 \text{ mA}$

- Current gain in common base mode ; $\alpha = \frac{I_C}{I_E}$

- Hence, $I_C = \alpha I_E = 0.95 \times 1 = 0.95 \text{ mA}$

- Also, $I_E = I_B + I_C$ (or) $I_B = I_E - I_C = 1 - 0.95 = 0.05 \text{ mA}$

6. In the circuit shown in the figure, the input voltage V_i is 20 V , $V_{BE} = 0 \text{ V}$ and $V_{CE} = 0 \text{ V}$. What are the values of I_B , I_C , β ?

Solution : $R_B = 500 \text{ k}\Omega$; $R_C = 4 \text{ k}\Omega$

- Voltage across R_B ; $V_B = V_i - V_{BE}$
 Since, $V_{BE} = 0 \text{ V}$ we have, $V_B = V_i$ Hence

$$I_B = \frac{V_B}{R_B} = \frac{V_i}{R_B} = \frac{20}{500 \times 10^3} = 0.04 \times 10^{-3}$$

$$I_B = 40 \times 10^{-6} \text{ A} = 40 \mu\text{A}$$

- Similarly, voltage across R_C ; $V_C = V_{CC} - V_{CE}$

Since, $V_{CE} = 0 \text{ V}$ we have, $V_C = V_{CC}$ Hence

$$I_C = \frac{V_C}{R_C} = \frac{V_{CC}}{R_C} = \frac{20}{4 \times 10^3} = 5 \times 10^{-3} = 5 \text{ mA}$$

- And current gain,



$$\beta = \frac{I_C}{I_B} = \frac{5 \times 10^{-3}}{40 \times 10^{-6}} = 0.125 \times 10^3 = 125$$

7. The current gain of a common emitter transistor circuit shown in figure is 120 . Draw the DC load line and mark the Q point on it. (V_{BE} to be ignored).


Solution : $\beta = 120$; $V_{CC} = 25 \text{ V}$; $R_B = 1 \text{ M}\Omega$;
 $R_C = 5 \text{ k}\Omega$

- Voltage across R_B ; $V_B = V_{CC} - V_{BE}$
 Since, $V_{BE} = 0 \text{ V}$ we have, $V_B = V_{CC}$ Hence
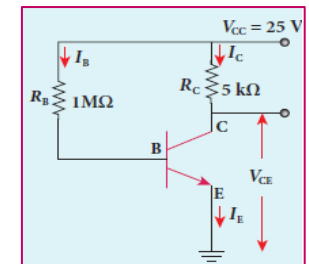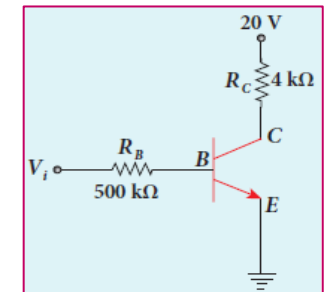
$$I_B = \frac{V_B}{R_B} = \frac{V_{CC}}{R_B} = \frac{25}{1 \times 10^6} = 25 \times 10^{-6} \text{ A} = 25 \mu\text{A}$$



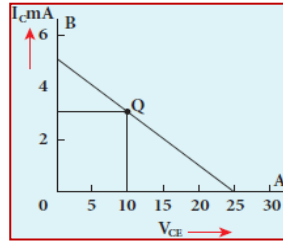- By definition, current gain ; $\beta = \frac{I_C}{I_B}$
- Hence collector current,
 $I_C = \beta I_B = 120 \times 25 \times 10^{-6} = 3000 \times 10^{-6} A$
 $I_C = 3 \times 10^{-3} A = 3 \text{ mA}$
- From figure, $V_{CE} = V_{CC} - V_C = V_{CC} - I_C R_C$
 $V_{CE} = 25 - (3 \times 10^{-3} \times 5 \times 10^3)$
 $V_{CE} = 25 - 15 = 10 \text{ V}$



8. Calculate the range of the variable capacitor that is to be used in a tuned-collector oscillator which has a fixed inductance of 150 μH . The frequency band is from 500 kHz to 1500 kHz.

Solution :

$L = 150 \mu H$

- Resonance frequency ; $f_o = \frac{1}{2\pi\sqrt{LC}}$ (or) $f_o^2 = \frac{1}{4\pi^2 LC}$
- Hence capacitance ; $C = \frac{1}{4\pi^2 L f_o^2}$
- When, $f_o = 500 \text{ kHz}$,

$$C = \frac{1}{4 \times (3.14)^2 \times 150 \times 10^{-6} \times (500 \times 10^3)^2}$$

$$C = \frac{1}{4 \times 9.8596 \times 150 \times 250000}$$

$$C = 6.761 \times 10^{-10} \text{ F} = 676.1 \times 10^{-12} \text{ F}$$

$$C \approx 676 \text{ pF}$$

- When, $f_o = 1500 \text{ kHz}$

$$C = \frac{1}{4 \times (3.14)^2 \times 150 \times 10^{-6} \times (1500 \times 10^3)^2}$$

$$C = \frac{1}{4 \times 9.8596 \times 150 \times 2250000}$$

$$C = 7.511 \times 10^{-11} \text{ F} = 75.11 \times 10^{-12} \text{ F}$$


$$C \approx 75 \text{ pF}$$

Therefore, the capacitor range is 75 pF – 676 pF

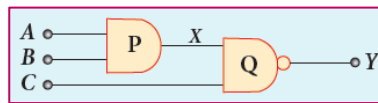9. What is the output Y in the following circuit, when all the three inputs A, B, and C are first 0 and then 1?

Solution :

- Out put of AND gate P : $X = A . B$
- Out put of NAND gate Q : $Y = \overline{X . B}$



A	B	C	$X = A . B$	$Y = \overline{X . B}$
0	0	0	0	1
1	1	1	1	0


No	Log
1	0.0000
4	0.6021
9.8596	0.9939
150	2.1761
250000	5.3979
(+)	9.1700
Nr	0.0000
Dr	9.1700
(-)	10.8300
ALog	6.761 $\times 10^{-10}$

No	Log
1	0.0000
4	0.6021
9.8596	0.9939
150	2.1761
2250000	6.3522
(+)	10.1243
Nr	0.0000
Dr	10.1243
(-)	11.8757
ALog	7.511 $\times 10^{-11}$

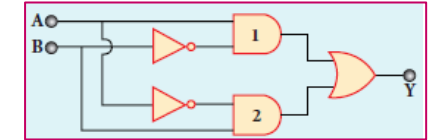10. In the combination of the following gates, write the Boolean equation for output Y in terms of inputs A and B.

Solution :

- The output at the 1st AND gate = $A . \overline{B}$
- The output at the 2nd AND gate = $\overline{A} . B$
- The output at the OR gate ; $Y = A . \overline{B} + \overline{A} . B$



11. Prove the Boolean identity $AC + ABC = AC$ and give its circuit description.

Solution :


$$AC + ABC = AC . (1 + B) \quad \text{[OR law-2]}$$

$$= AC . 1 \quad \text{[AND law - 2]}$$


$$AC + ABC = AC$$

- Thus the Boolean identity is proved.

Circuit description:

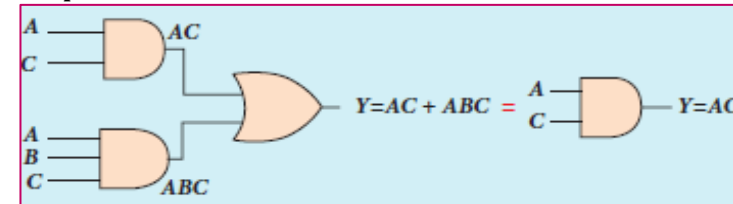

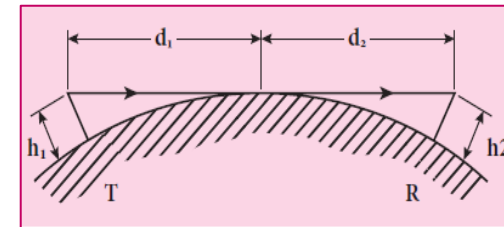12. A transmitting antenna has a height of 40 m and the height of the receiving antenna is 30 m. What is the maximum distance between them for line-of-sight communication? The radius of the earth is $6.4 \times 10^6 \text{ m}$.



Solution :

- The total distance d between the transmitting and receiving antennas will be the sum of the individual distances of coverage.

$$d = d_1 + d_2 = \sqrt{2R h_1} + \sqrt{2R h_2} = \sqrt{2R} (\sqrt{h_1} + \sqrt{h_2})$$

$$d = \sqrt{2 \times 6.4 \times 10^6} (\sqrt{40} + \sqrt{30})$$

$$d = \sqrt{2 \times 6.4 \times 10^6} \times \sqrt{10} (\sqrt{4} + \sqrt{3})$$

$$d = \sqrt{2 \times 6.4 \times 10^7} (\sqrt{4} + \sqrt{3})$$

$$d = \sqrt{2 \times 64 \times 10^6} (\sqrt{4} + \sqrt{3})$$

$$d = 1.414 \times 8 \times 10^3 (2 + 1.732)$$


$$d = 1.414 \times 8 \times 10^3 \times 3.732$$

$$d = 42.21 \times 10^3 \text{ m} = 42.21 \text{ km}$$

No	Log
1.414	0.1504
8	0.9031
3.732	0.5719
(+)	1.6254
ALog	4.221 $\times 10^4$

EXERCISE PROBLEMS

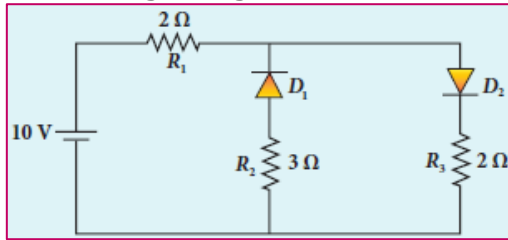1. The given circuit has two ideal diodes connected as shown in figure below. Calculate the current flowing through the resistance R_1 .



Solution :

- Here diode D_1 is reverse biased. So it acts as open switch (OFF) and hence it does not allow current to pass through it.
- But diode D_2 is forward biased. So it acts as closed switch (ON) and hence it allows current to pass through it.
- From Ohm's law, $V = I R_S$

$$(or) \quad I = \frac{V}{R_S} = \frac{10}{(2 + 2)} = \frac{10}{4} = 2.5 \text{ A}$$

2. Four silicon diodes and a 10Ω resistor are connected as shown in figure below. Each diode has a resistance of 1Ω . Find the current flows through the 10Ω resistor.

Solution :

- Here diode D_1 & D_4 is reverse biased. So it acts as open switch (OFF) and hence it does not allow current to pass through it.
- But diode D_2 & D_3 is forward biased. So it acts as closed switch (ON) and hence it allows current to pass through it.
- Hence the given circuit is simplified as shown.
- Since the barrier voltage of silicon is 0.7 V and hence voltage across 10Ω resistor,



$$V_{10} = 3 - 0.7 - 0.7 = 1.6 \text{ V}$$

- Total resistance of the circuit,

$$R_S = 1 + 10 + 1 = 12 \Omega$$

- Then the current through 10Ω resistor,
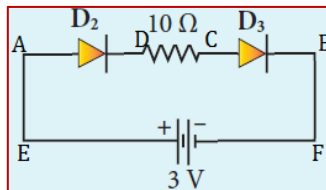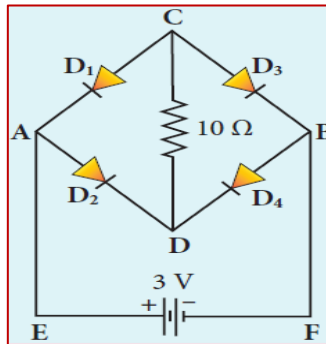
$$I = \frac{V_{10}}{R_S} = \frac{1.6}{12} = 0.133 \text{ A}$$




3. Assuming $V_{CEsat} = 0.2 \text{ V}$ and $\beta = 50$, find the minimum base current (I_B) required to drive the transistor given in the figure to saturation.

Solution : $V_{CC} = 3 \text{ V}$; $R_C = 1 \text{ k}\Omega = 1000 \Omega$

- From figure, $V_{CC} = I_C R_C + V_{CE}$
(or) $I_C R_C = V_{CC} - V_{CE}$
(or) $I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{3 - 0.2}{1000}$
 $I_C = 2.8 \times 10^{-3} \text{ A}$

- Then current gain ; $\beta = \frac{I_C}{I_B}$. Hence,
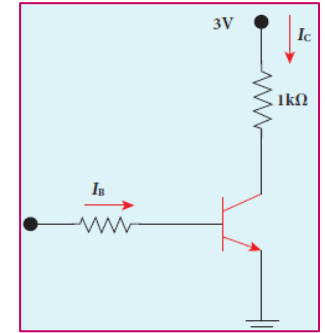
$$I_B = \frac{I_C}{\beta} = \frac{2.8 \times 10^{-3}}{50} = 0.056 \times 10^{-3} \text{ A} = 56 \times 10^{-6} = 56 \mu \text{ A}$$



4. A transistor of $\alpha = 0.99$ and $V_{BE} = 0.7 \text{ V}$ is connected in the common emitter configuration as shown in the figure. If the transistor is in saturation region, find the value of collector current.

Solution :

- If $\alpha = 0.99$ then,
 $\beta = \frac{\alpha}{1 - \alpha} = \frac{0.99}{1 - 0.99} = \frac{0.99}{0.01} = 99$

- By definition, current gain,

$$\beta = \frac{I_C}{I_B} \quad (or) \quad I_B = \frac{I_C}{\beta} = \frac{I_C}{90}$$

- Here one thing must be remember that, transistor in saturation region have, $V_{BE-sat} = 0.8 \text{ V}$ and $V_{CE-sat} = 0.2 \text{ V}$

- From figure, for input applying Kirchoff's voltage law

$$\begin{aligned} V_1 + V_2 + V_3 &= V_{CC} - V_{BE-sat} \\ 1000(I_C + I_B) + 10000 I_B + 1000(I_C + I_B) &= 12 - 0.8 \\ 2000 I_C + 12000 I_B &= 11.2 \quad \text{----- (1)} \end{aligned}$$


- Similarly for output applying Kirchoff's voltage law

$$\begin{aligned} V_1 + V_2 + V_3 &= V_{CC} - V_{CE-sat} \\ 1000(I_C + I_B) + 10000 I_B + 1000(I_C + I_B) &= 12 - 0.2 \\ 3000 I_C + 2000 I_B &= 11.8 \quad \text{----- (2)} \end{aligned}$$

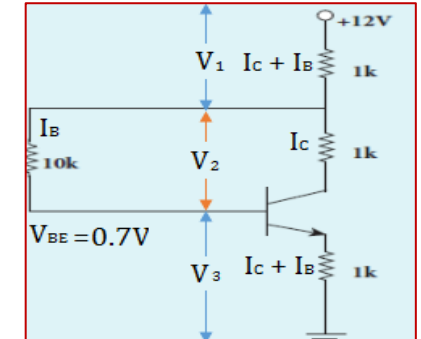- (2) X 6 \Rightarrow $18000 I_C + 12000 I_B = 70.8$ ----- (3)


$$\begin{aligned} (3) - (1) &\Rightarrow 16000 I_C = 59.6 \\ I_C &= \frac{59.6}{16000} = 3.724 \times 10^{-3} \text{ A} \end{aligned}$$

$$I_C = 3.724 \times 10^{-3} \text{ A} = 3.724 \text{ mA}$$



No	Log
59.6	1.7752
16000	4.2041
(-)	$\bar{3}.5711$
ALog	3.724×10^{-3}

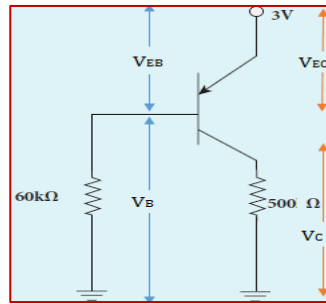5. In the circuit shown in the figure, the BJT has a current gain (β) of 50. For an emitter - base voltage $V_{EB} = 600 \text{ mV}$, calculate the emitter - collector voltage V_{EC} (in volts).




Solution : $V_E = 3 \text{ V}$; $R_B = 60\text{k}\Omega$; $R_C = 500 \Omega$

From figure,, $V_E = V_{EB} + V_B$
 (or) $V_B = V_E - V_{EB}$
 $60000 I_B = 3 - 600 \times 10^{-3}$
 $60 \times 10^3 I_B = 3 - 0.6 = 2.4$
 $I_B = \frac{2.4}{60 \times 10^3} = 0.04 \times 10^{-3} \text{ A}$
 $= 40 \times 10^{-6} \text{ A} = 40 \mu \text{ A}$

By definition, current gain $\beta = \frac{I_C}{I_B}$
 (or) $I_C = \beta I_B = 50 \times 40 \times 10^{-6} = 2000 \times 10^{-6} \text{ A} = 2 \times 10^{-3} = 2 \text{ mA}$
 Hence, $V_{EC} = V_E - V_C = V_E - I_C R_C = 3 - (2 \times 10^{-3} \times 0.5 \times 10^3)$
 $V_{EC} = 3 - 1 = 2 \text{ V}$

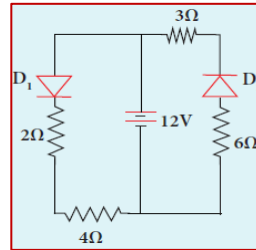6. Determine the current flowing through 3Ω and 4Ω resistors of the circuit given below. Assume that diodes D_1 and D_2 are ideal diodes.



- Solution :**
- Here diode D_1 is forward biased (closed switch) and D_2 is reverse biased (open switch)
 - So D_1 conducts while D_2 do not conduct the current.
 - For ideal diode, there is no barrier voltage (i.e.) $V_B = 0$
 - Let 'I' be the current through D_1 , then by Ohm's Kirchoff's voltage law,
 $2I + 4I = 12$ (or) $6I = 12$ (or) $I = 2 \text{ A}$
 - Since D_2 will not conduct, no current flows through diode D_2
 - Thus current flowing through 3Ω and 4Ω resistors of the circuit are **0 and 2 A** Respectively.

7. Prove the following Boolean expressions using the laws and theorems of Boolean algebra. (i) $(A+B)(A+\bar{B}) = A$ (ii) $A(\bar{A}+B) = AB$ (iii) $(A+B)(A+C) = A+BC$

Solution :

(i) $(A+B)(A+\bar{B}) = AA + A\bar{B} + BA + B\bar{B}$ [By AND laws; $AA = A$ & $B\bar{B} = 0$]
 $= A + A(\bar{B} + B) + 0$ [By OR laws ; $\bar{B} + B = 1$ & $A + 0 = A$]
 $= A + A(1)$ [By AND laws ; $A \cdot 1 = A$]
 $(A+B)(A+\bar{B}) = A$ [By OR laws ; $A + A = A$]

(ii) $A(\bar{A} + B) = A\bar{A} + AB$ [By AND laws ; $A\bar{A} = 0$]
 $= 0 + AB$ [By OR laws ; $0 + A = A$]
 $A(\bar{A} + B) = AB$


(iii) $(A+B)(A+C) = AA + AC + BA + BC$
 $= A + AC + BA + BC$
 $= A(1 + C + B) + BC$ [By OR laws ; $1 + A = 1$]
 $= A(1) + BC$
 $(A+B)(A+C) = A + BC$

8. Verify the given Boolean equation $A + \bar{A}B = A + B$ using truth table.

Solution :

A	B	\bar{A}	$\bar{A}B$	$A + \bar{A}B$	$A + B$
0	0	1	0	0	0
0	1	1	1	1	1
1	0	0	0	1	1
1	1	0	0	1	1

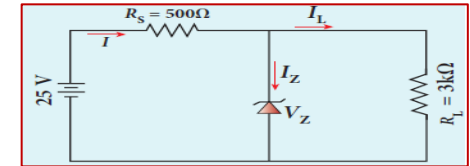9. In the given figure of a voltage regulator, a Zener diode of breakdown voltage 15V is employed. Determine the current through the load resistance, the total current and the current through the diode. Use diode approximation.




Solution : $V = 25 \text{ V}$; $R_S = 500 \Omega$; $V_Z = 15 \text{ V}$; $R_L = 3 \text{ k}\Omega = 3000 \Omega$

- From the figure, $V_{R_S} = V - V_Z = 25 - 15 = 10 \text{ V}$
- From Ohm's law Current through load resistance R_L ,
 $I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \frac{15}{3000} = 5 \times 10^{-3} \text{ A} = 5 \text{ mA}$
- And, current through R_S (i.e.) total current
 $I = \frac{V_{R_S}}{R_S} = \frac{10}{500} = \frac{1}{50} = 0.02 \text{ A} = 20 \times 10^{-3} \text{ A} = 20 \text{ mA}$
- If I_Z be the current through Zener diode, then from Kirchoff's current law,
 $I = I_L + I_Z$
 (or) $I_Z = I - I_L = (20 \times 10^{-3}) - (5 \times 10^{-3}) = 15 \times 10^{-3} \text{ A}$
 $I_Z = 15 \text{ mA}$

10. Write down Boolean equation for the output Y of the given circuit and give its truth table.

Solution :

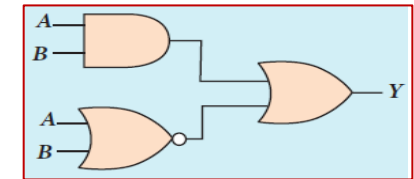

- Output of AND gate = $A \cdot B$
- Output of NOR gate = $\bar{A} + \bar{B}$
- Thus the final output of OR gate ;

$$Y = (A \cdot B) + (\bar{A} + \bar{B})$$

A	B	$A \cdot B$	$A + B$	$\bar{A} + \bar{B}$	$Y = (A \cdot B) + (\bar{A} + \bar{B})$
0	0	0	0	1	1
0	1	0	1	0	1
1	0	0	1	0	1
1	1	1	1	0	1