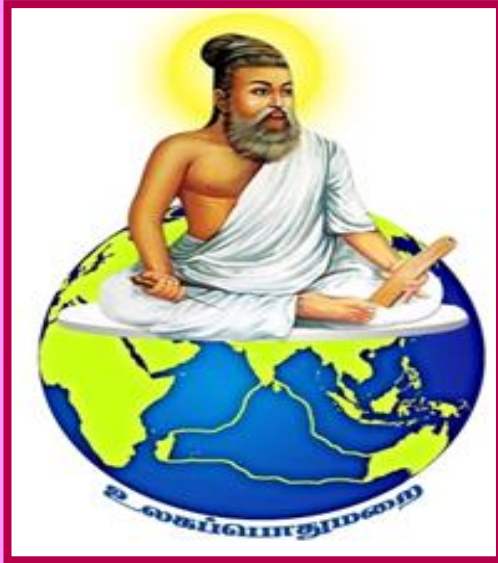


**HIGHER SECONDARY
SECOND YEAR**

PHYSICS

**UNIT -2
CURRENT ELECTRICITY**

PROBLEMS AND SOLUTIONS



victory R. SARAVANAN. M.Sc, M.Phil, B.Ed
PG ASST (PHYSICS)
GBHSS, PARANGIPETTAI - 608 502

EXAMPLE PROBLEMS

1. Compute the current in the wire if a charge of 120 C is flowing through a copper wire in 1 minute.

Solution :- $t = 1 \text{ min} = 60 \text{ s}$; $q = 120 \text{ C}$; $I = ?$

◆ By definition, electric current (i.e.) rate of flow of charge is given by,

$$I = \frac{q}{t} = \frac{120}{60} = 2 \text{ A}$$

2. If an electric field of magnitude 570 N C⁻¹, is applied in the copper wire, find the acceleration experienced by the electron.

Solution :- $E = 570 \text{ N C}^{-1}$; $e = 1.6 \times 10^{-19} \text{ C}$; $m = 9.1 \times 10^{-31} \text{ kg}$; $a = ?$

◆ From Newton's second law, force is given by ; $F = ma$

◆ Hence the acceleration,

$$a = \frac{F}{m} = \frac{eE}{m} = \frac{1.6 \times 10^{-19} \times 570}{9.1 \times 10^{-31}} = \frac{912}{9.1} \times 10^{12} = 100.1 \times 10^{12}$$

$$a = 1.001 \times 10^{14} \text{ m s}^{-2}$$

3. A copper wire of cross-sectional area 0.5 mm² carries a current of 0.2 A. If the free electron density of copper is 8.4 × 10²⁸ m⁻³ then compute the drift velocity of free electrons.

Solution :- $A = 0.5 \text{ mm}^2 = 0.5 \times 10^{-6} \text{ m}^2$; $I = 0.2 \text{ A}$; $n = 8.4 \times 10^{28} \text{ m}^{-3}$

◆ The relation between drift velocity of electrons and current in a wire of cross-sectional area A is ; $I = nAev_d$

◆ Hence, the drift velocity ; $v_d = \frac{I}{nAe}$

$$v_d = \frac{0.2}{8.4 \times 10^{28} \times 0.5 \times 10^{-6} \times 1.6 \times 10^{-19}} = \frac{0.2 \times 10^{-3}}{6.72}$$

$$v_d = 2.976 \times 10^{-2} \times 10^{-3} = 2.976 \times 10^{-5} \text{ m s}^{-1}$$

$$v_d = 0.02976 \times 10^{-3} \text{ m s}^{-1} \approx 0.03 \times 10^{-3} \text{ m s}^{-1}$$

No	Log
0.2	1.3010
6.72	0.8274
(-)	2.4736
A Log	2.976 × 10 ⁻²

4. Determine the number of electrons flowing per second through a conductor, when a current of 32 A flows through it.

Solution :- $I = 32 \text{ A}$; $t = 1 \text{ s}$; $e = 1.6 \times 10^{-19}$; $n = ?$

◆ By definition, current (rate of flow of charge) is given by ; $I = \frac{q}{t} = \frac{ne}{t}$

◆ Hence the number of electrons flowing per second ;

$$n = \frac{It}{e} = \frac{32 \times 1}{1.6 \times 10^{-19}} = 20 \times 10^{19} = 2 \times 10^{20} \text{ electrons}$$


5. A potential difference across 24 Ω resistor is 12 V. What is the current through the resistor?

Solution :- $R = 24 \Omega$; $V = 12 \text{ V}$; $I = ?$

◆ From Ohm's law;

$$I = \frac{V}{R} = \frac{12}{24} = \frac{1}{2}$$

$$I = 0.5 \text{ A}$$

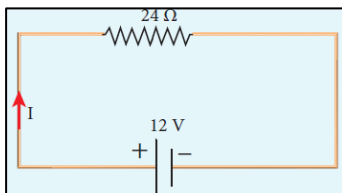

6. The resistance of a wire is 20 Ω. What will be new resistance, if it is stretched uniformly 8 times its original length?

Solution :- $R_1 = 20 \Omega$; $l_1 = l$; $l_2 = 8l$; $R_2 = ?$

◆ Though the wire is stretched, its volume remains unchanged.(i.e.)

Initial volume = final volume

$$A_1 l_1 = A_2 l_2$$

$$A_1 l = A_2 (8l)$$

$$\frac{A_2}{A_1} = \frac{1}{8} \text{ ----- (1)}$$

◆ Initial resistance ; $R_1 = \rho \frac{l_1}{A_1}$


◆ New resistance ; $R_2 = \rho \frac{l_2}{A_2}$

◆ Hence the ratio ; $\frac{R_1}{R_2} = \frac{l_1 A_2}{A_1 l_2} = \frac{A_1 l_1}{A_1 l_2} = \frac{1}{8} \times \frac{l}{8l} = \frac{1}{64}$

$$\therefore R_2 = 64 R_1 = 64 \times 20 = 1280 \Omega$$

◆ Hence, stretching the length of the wire has increased its resistance.

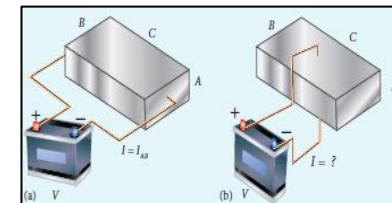7. Consider a rectangular block of metal of height A, width B and length C as shown in the figure. If a potential difference of V is applied between the two faces A and B of the block [figure (a)], the current I_{AB} is observed. Find the current that flows if the same potential difference V is applied between the two faces B and C of the block [figure (b)]. Give your answers in terms of I_{AB} .



Solution :-

◆ In first case ; length =C and area = AB. Hence resistance and current

$$R_{AB} = \rho \frac{\text{length}}{\text{area}} = \rho \frac{C}{AB}$$

$$I_{AB} = \frac{V}{R_{AB}} = \frac{V}{\left[\rho \frac{C}{AB} \right]} = \frac{V (AB)}{\rho C} \text{ ----- (1)}$$

◆ In second case ; length =A and area = BC. Hence resistance and current

$$R_{BC} = \rho \frac{\text{length}}{\text{area}} = \rho \frac{A}{BC}$$

$$I_{BC} = \frac{V}{R_{BC}} = \frac{V}{\left[\rho \frac{A}{BC} \right]} = \frac{V (BC)}{\rho A} \text{ ----- (2)}$$


◆ Divide equation (2) by (1), we get

$$\frac{I_{BC}}{I_{AB}} = \frac{[V (BC)/\rho A]}{[V (AB)/\rho C]} = \frac{V (BC)}{\rho A} \times \frac{\rho C}{V (AB)} = \frac{C^2}{A^2}$$

$$I_{BC} = \frac{C^2}{A^2} I_{AB}$$

◆ Since $C > A$, the current $I_{BC} > I_{AB}$

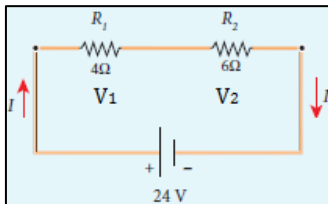8. Calculate the equivalent resistance for the circuit which is connected to 24 V battery and also find the potential difference across each resistor in the circuit.



Solution :- $R_1 = 4 \Omega ; R_2 = 6 \Omega ; V = 24 V$

◆ Effective resistance in series circuit,

$$R_S = R_1 + R_2 = 4 + 6 = 10 \Omega$$


◆ From Ohm's law, current in the circuit ; $I = \frac{V}{R_S} = \frac{24}{10} = 2.4 A$

◆ Hence voltage across the resistors,

$$V_1 = I R_1 = 2.4 \times 4 = 9.6 V$$

$$V_2 = I R_2 = 2.4 \times 6 = 14.4 V$$

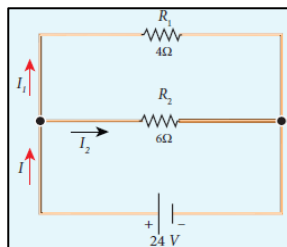9. Calculate the equivalent resistance in the following circuit and also find the values of current I, I_1 and I_2 in the given circuit.



Solution :- $R_1 = 4 \Omega ; R_2 = 6 \Omega ; V = 24 V$

◆ Effective resistance in parallel circuit,

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{4} + \frac{1}{6} = \frac{6+4}{24} = \frac{10}{24} = \frac{1}{2.4}$$

(or) $R_p = 2.4 \Omega$

◆ Then current flows through the resistors,

$$I_1 = \frac{V}{R_1} = \frac{24}{4} = 6 A$$

$$I_2 = \frac{V}{R_2} = \frac{24}{6} = 4 A$$

◆ The current I is the sum of the currents in the two branches. Then

$$I = I_1 + I_2 = 6 + 4 = 10 A$$

10. Two resistors when connected in series and parallel, their equivalent resistances are 15Ω and $\frac{56}{15} \Omega$ respectively. Find the values of the resistances.

Solution :- $R_S = 15 \Omega ; R_p = \frac{56}{15} \Omega ; R_1 = ? ; R_2 = ?$

◆ Effective resistance in series circuit ; $R_S = R_1 + R_2$

$$15 = R_1 + R_2 \quad \text{----- (1)}$$

◆ Effective resistance in parallel circuit ; $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2}$

$$\frac{15}{56} = \frac{R_1 + R_2}{R_1 R_2} = \frac{15}{R_1 R_2} \quad [\because \text{by eqn (1)}]$$

$$\therefore 56 = R_1 R_2 \quad \text{----- (2)}$$


◆ From equation (1) & (2) ; $R_1 + R_2 = 15$ and $R_1 R_2 = 56$, we get

$$R_1 = 7 \text{ \& } R_2 = 8 \text{ (or) } R_1 = 8 \text{ \& } R_2 = 7$$

◆ If $R_1 = 7$ then, $R_2 = 15 - R_1 = 15 - 7 = 8$. So $R_1 = 7 \Omega ; R_2 = 8 \Omega$

◆ If $R_1 = 8$ then, $R_2 = 15 - R_1 = 15 - 8 = 7$. So $R_1 = 8 \Omega ; R_2 = 7 \Omega$

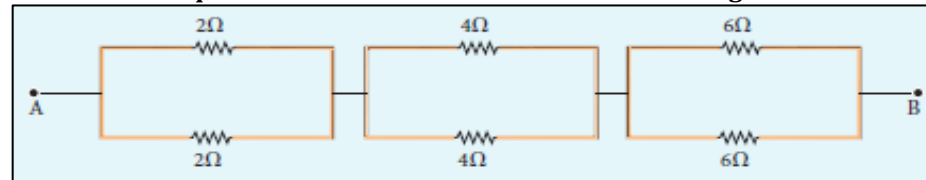11. Calculate the equivalent resistance between A and B in the given circuit.



Solution :- $R_{AB} = ?$


◆ Here, 2Ω and 2Ω , 4Ω and 4Ω , 6Ω and 6Ω are in parallel, then

$$\frac{1}{R_{P1}} = \frac{1}{2} + \frac{1}{2} = 1 \text{ (or) } R_{P1} = 1 \Omega$$

$$\frac{1}{R_{P2}} = \frac{1}{4} + \frac{1}{4} = \frac{1}{2} \text{ (or) } R_{P2} = 2 \Omega$$

$$\frac{1}{R_{P3}} = \frac{1}{6} + \frac{1}{6} = \frac{2}{6} \text{ (or) } R_{P3} = \frac{6}{2} = 3 \Omega$$


◆ Thus the above circuit becomes,

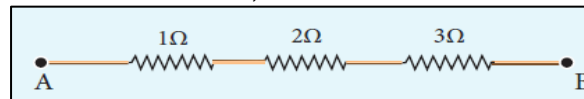

◆ Here, 1Ω , 2Ω and 3Ω are in series, then the effective resistance becomes,

$$R_{AB} = R_{P1} + R_{P2} + R_{P3} = 1 + 2 + 3$$

$$R_{AB} = 6 \Omega$$

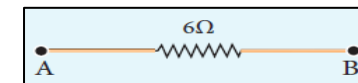



12. Five resistors are connected in the configuration as shown in the figure. Calculate the equivalent resistance between the points a and b.

Solution :-

◆ Let us assume that a current is entering the junction at a.

◆ Since all the resistances in the outside loop are the same (1Ω), the current in the branches ac and ad must be equal. Hence the points C and D are at the same potential and no current through 5Ω .

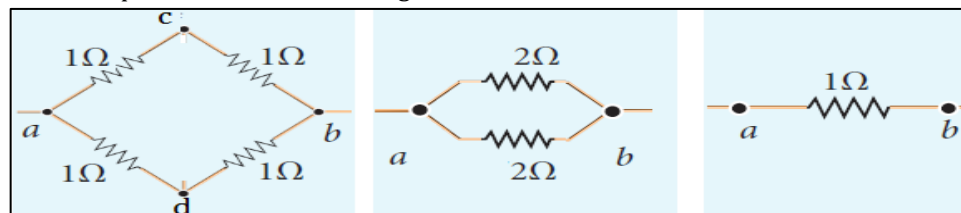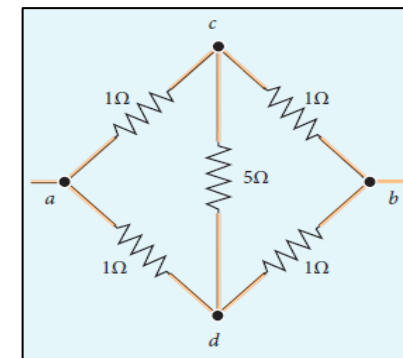◆ It implies that the 5Ω has no role in determining the equivalent resistance and it can be removed. So the circuit is simplified as shown in the figure.



- Effective resistance in series connection is,

$$R_{S1} = R_{ac} + R_{cb} = 1 + 1 = 2 \Omega$$

$$R_{S2} = R_{ad} + R_{db} = 1 + 1 = 2 \Omega$$

- Effective resistance in parallel connection is,

$$\frac{1}{R_{ab}} = \frac{1}{R_{S1}} + \frac{1}{R_{S2}} = \frac{1}{2} + \frac{1}{2} = 1$$

$$R_{ab} = 1 \Omega$$

13. If the resistance of coil is 3Ω at 200°C and $\alpha = 0.004/^\circ\text{C}$ then determine its resistance at 100°C .

Solution :- $T_o = 20^\circ\text{C}$; $T = 100^\circ\text{C}$; $R_o = 3 \Omega$; $R_T = ?$

- Resistance at $T^\circ\text{C}$; $R_T = R_o [1 + \alpha (T - T_o)]$

$$R_T = 3 [1 + 0.004 (100 - 20)] = 3 [1 + 0.004 \times 80]$$

$$R_T = 3 [1 + 0.32] = 3 \times 1.32$$

$$R_T = 3.96 \Omega$$

14. Resistance of a material at 20°C and 40°C are 45Ω and 85Ω respectively. Find its temperature coefficient of resistivity.

Solution :- $T_o = 20^\circ\text{C}$; $T = 40^\circ\text{C}$; $R_o = 45 \Omega$; $R_T = 85 \Omega$; $\alpha = ?$

- The temperature coefficient of resistivity is

$$\alpha = \frac{1}{R_o} \frac{\Delta R}{\Delta T} = \frac{1}{R_o} \frac{(R_T - R_o)}{(T - T_o)}$$

$$\alpha = \frac{1}{45} \times \frac{(85 - 45)}{(40 - 20)} = \frac{1}{45} \times \frac{40}{20} = \frac{1}{45} \times 2$$

$$\alpha = 0.044 / ^\circ\text{C}$$

15. A battery of voltage V is connected to 30 W bulb and 60 W bulb as shown in the figure. (a) Identify brightest bulb (b) which bulb has greater resistance? (c) Suppose the two bulbs are connected in series, which bulb will glow brighter?

Solution :- $P_1 = 30 \text{ W}$; $P_2 = 60 \text{ W}$


- (a) The power delivered by the battery ; $P = VI$.

Since the bulbs are connected in parallel, the voltage drop across each bulb is the same. If the voltage is kept fixed, then the power is directly proportional to current ($P \propto I$). Since $P_1 < P_2$, we have $I_1 < I_2$. So 60 W bulb draws twice as much as current as 30 W and hence **60 W bulb will glow brighter than 30 W bulb.**

- (b) The power delivered by the battery ; $P = VI = \frac{V^2}{R}$. Hence $P \propto \frac{1}{R}$

Since $P_1 < P_2$, we have $R_1 > R_2$. It implies that, the **30W has twice as much as resistance as 60 W bulb.**

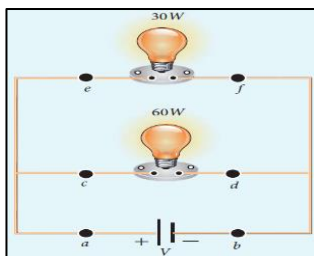- (c) When the bulbs are connected in series, the current passing through each bulb is the same. It is equivalent to two resistors connected in series. The bulb which has higher resistance has higher voltage drop. So **30W bulb will glow brighter than 60W bulb.** So the higher power rating does not always imply more brightness and it depends whether bulbs are connected in series or parallel.



16. Two electric bulbs marked $20 \text{ W} - 220 \text{ V}$ and $100 \text{ W} - 220 \text{ V}$ are connected in series to 440 V supply. Which bulb will get fused?

Solution :-

- To check which bulb will get fused, the voltage drop across each bulb has to be calculated.

- The power delivered by the battery ; $P = VI = \frac{V^2}{R}$

- Hence the resistance of the bulbs,

$$R_1 = \frac{V_1^2}{P_1} = \frac{220^2}{20} = \frac{48400}{20} = 2420 \Omega$$

$$R_2 = \frac{V_2^2}{P_2} = \frac{220^2}{100} = \frac{48400}{100} = 484 \Omega$$

- The two bulbs are connected in series, effective resistance

$$R_{tot} = 2420 + 484 = 2904 \Omega$$

- When the bulbs are connected in series, the current passing through each bulb is the same and it is given by,

$$I = \frac{V}{R_{tot}} = \frac{V_1 + V_2}{R_{tot}} = \frac{220 + 220}{2904} = \frac{440}{2904} \text{ A}$$

$$I = 1.515 \times 10^{-1} \text{ A} = 0.1515 \text{ A}$$

- The voltage drop across the 20 W bulb is

$$V_1 = IR_1 = 0.1515 \times 2420 = 3.667 \times 10^2 = 366.7 \text{ V}$$

- The voltage drop across the 100 W bulb is

$$V_2 = 0.1515 \times 484 = 7.333 \times 10^1 = 73.33 \text{ V}$$

- The 20 W bulb will get fused** because the voltage across it is more than the voltage rating.

17. A battery has an emf of 12 V and connected to a resistor of 3Ω . The current in the circuit is 3.93 A . Calculate (a) terminal voltage and the internal resistance of the battery (b) power delivered by the battery and power delivered to the resistor

Solution :- $I = 3.93 \text{ A}$; $\epsilon = 12 \text{ V}$; $R = 3 \Omega$

- (a) The terminal voltage of the battery is equal to voltage drop across the resistor

$$V = IR = 3.93 \times 3 = 11.79 \text{ V}$$

Internal resistance of the battery,

$$r = \left[\frac{\epsilon - V}{I} \right] R = \left[\frac{12 - 11.79}{3.93} \right] \times 3$$

$$r = \frac{0.21 \times 3}{3.93} = \frac{0.63}{3.93} = 5.341 \times 10^{-2} \Omega = 0.05341 \Omega$$


- (b) The power delivered by the battery,

$$P = \epsilon I = 12 \times 3.93 = 47.16 \text{ W}$$

The power delivered to the resistor

$$P = VI = 11.79 \times 3.93 = 46.33 \text{ W}$$

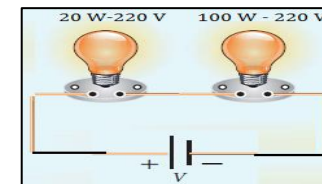The remaining power $P = 47.16 - 46.33 = 0.83 \text{ W}$ is delivered to the internal resistance and cannot be used to do useful work. (It is equal to $I^2 r$).



No	Log
440	2.6435
2904	3.4630

(-) A Log	1.1805 1.515 X 10 ⁻¹
--------------	------------------------------------

No	Log
0.1515	1.1805
2420	3.3838


(+) A Log	2.5643 3.667 X 10 ²
--------------	-----------------------------------

No	Log
0.1515	1.1805
484	2.6848

(+) A Log	1.8653 7.333 X 10 ¹
--------------	-----------------------------------

18. From the given circuit, Find

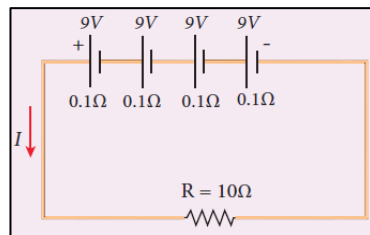- (a) Equivalent emf of the combination
- (b) Equivalent internal resistance
- (c) Total current
- (d) Potential difference across external resistance
- (e) Potential difference across each cell



Solution :- $n = 4$; $\epsilon = 9V$; $r = 0.1\Omega$

- (a) Equivalent emf of the combination ; $\epsilon_{tot} = n \epsilon = 4 \times 9 = 36V$
- (b) Equivalent internal resistance ; $r_{tot} = nr = 4 \times 0.1 = 0.4\Omega$
- (c) Total current ;

$$I = \frac{n \epsilon}{R + nr} = \frac{4 \times 9}{10 + 4 \times 0.1}$$


$$I = \frac{36}{10 + 0.4} = \frac{36}{10.4} = 3.462A$$

No	Log
36	1.5563
10.4	1.0170
(-)	0.5393
ALog	3.462×10^0

- (d) Potential difference across external resistance ; $V = IR = 3.462 \times 10 = 34.62V$
- (e) Potential difference across each cell ; $v = \frac{V}{4} = \frac{34.62}{4} = 8.655V$

19. From the given circuit. Find

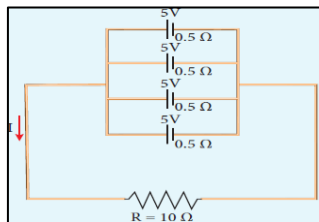- (a) Equivalent emf
- (b) Equivalent internal resistance
- (c) Total current (I)
- (d) Potential difference across each cell
- (e) Current from each cell



Solution :-

- (a) Equivalent emf ; $\epsilon_{tot} = \epsilon = 5V$
- (b) Equivalent internal resistance ; $r_{tot} = \frac{r}{n} = \frac{0.5}{4} = 0.125\Omega$

- (c) Total current ; $I = \frac{\epsilon}{R + \frac{r}{n}} = \frac{5}{10 + \frac{0.5}{4}}$

$$I = \frac{5}{10 + 0.125} = \frac{5}{10.125}$$

$$I = 4.939 \times 10^{-1} A = 0.4939A \approx 0.5A$$

No	Log
5	0.6990
10.125	1.0054
(-)	1.6936
ALog	4.939×10^{-1}


- (d) Potential difference across each cell ; $V = IR = 0.5 \times 10 = 5V$

- (e) Current from each cell ; $I^1 = \frac{I}{n} = \frac{0.5}{4} = 0.125A$

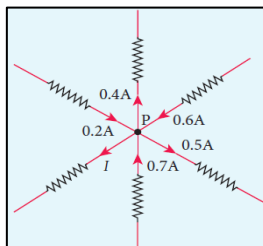20. For the given circuit find the value of I.

Solution :-


- From Kirchoff's first law, at junction P ; $\sum I = 0$
- $$0.2 + (-0.4) + 0.6 + (-0.5) + 0.7 + (-I) = 0$$
- $$0.2 - 0.4 + 0.6 - 0.5 + 0.7 - I = 0$$
- $$\therefore I = 0.2 - 0.4 + 0.6 - 0.5 + 0.7$$
- $$I = 1.5 - 0.9 = 0.6A$$




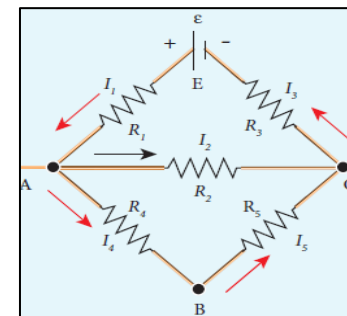
21. The following figure shows a complex network of conductors which can be divided into two closed loops like EACE and ABCA.

Solution :-

- Apply Kirchoff's voltage rule (KVR) in EACE
- $$\sum IR = \sum \epsilon$$
- $$I_1 R_1 + I_2 R_2 + I_3 R_3 = \epsilon$$
- Apply Kirchoff's voltage rule (KVR) in ABCA
- $$\sum IR = \sum \epsilon$$
- $$I_4 R_4 + I_5 R_5 - I_3 R_3 = 0$$



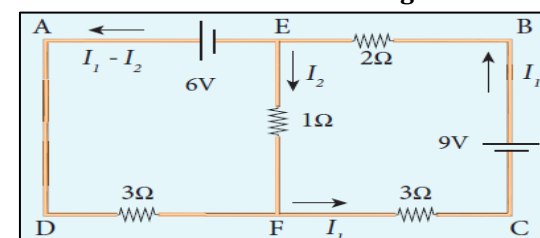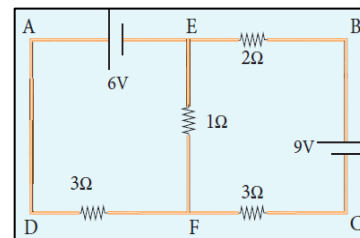22. Calculate the current that flows in the 1Ω resistor in the following circuit.



Solution :-

- We can denote the current that flows from 9V battery as I_1 and it splits up into I_2 and $(I_1 - I_2)$ at the junction E according Kirchoff's current rule (KCR).

- Now consider the loop EADFE and apply KVR, we get

$$\sum IR = \sum \epsilon$$

$$3(I_1 - I_2) - I_2 = 6$$

$$3I_1 - 3I_2 - I_2 = 6$$

$$3I_1 - 4I_2 = 6 \quad \text{----- (1)}$$

- Now consider the loop EFCBE and apply KVR, we get

$$\sum IR = \sum \epsilon$$

$$I_2 + 3I_1 + 2I_1 = 9$$

$$5I_1 + I_2 = 9 \quad \text{----- (2)}$$

$$(2) \times 4 \Rightarrow 20I_1 + 4I_2 = 36 \quad \text{----- (3)}$$

- (1) + (3) \Rightarrow

$$23I_1 = 42$$

$$I_1 = \frac{42}{23} = 1.826A$$

- Put, $I_1 = 1.826$ in equation (1)

$$3(1.826) - 4I_2 = 6$$

$$5.478 - 4I_2 = 6$$

$$-4I_2 = 6 - 5.478 = 0.522$$

$$(or) 4I_2 = -0.522$$

$$I_2 = -\frac{0.522}{4} = -0.1305A$$

- It implies that the current in the 1Ω resistor flows from F to E.

23. In a Wheatstone's bridge $P = 100 \Omega$, $Q = 1000 \Omega$ and $R = 40 \Omega$. If the galvanometer shows zero deflection, determine the value of S .

Solution :-

- From the balanced condition of Wheatstone's bridge,

$$\frac{P}{Q} = \frac{R}{S}$$

$$S = \frac{R Q}{P} = \frac{40 \times 1000}{100} = 400 \Omega$$

24. What is the value of x when the Wheatstone's network is balanced?

Solution :- $P = 500 \Omega$, $Q = 800 \Omega$, $R = x + 400$, $S = 1000 \Omega$

- From the balanced condition of Wheatstone's bridge,

$$\frac{P}{Q} = \frac{R}{S}$$

$$\frac{500}{800} = \frac{x + 400}{1000}$$


$$\frac{5}{8} = \frac{x + 400}{1000}$$

$$5000 = 8(x + 400)$$

$$5000 = 8x + 3200$$

$$8x = 5000 - 3200 = 1800$$

$$x = \frac{1800}{8} = 225 \Omega$$

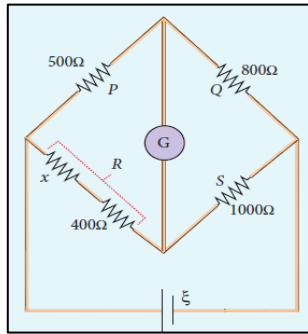

25. In a meter bridge experiment with a standard resistance of 15Ω in the right gap, the ratio of balancing length is 3:2. Find the value of the other resistance.

Solution :- $Q = 15 \Omega$; $l_1 : l_2 = 3 : 2$; $P = ?$

- From the theory of meter bridge ; $\frac{P}{Q} = \frac{l_1}{l_2}$
- (or) $P = Q \frac{l_1}{l_2} = 15 \times \frac{3}{2} = \frac{45}{2}$
- $P = 22.5 \Omega$

26. In a meter bridge experiment, the value of resistance box connected in the right gap is 10Ω . The balancing length is $l_1 = 55 \text{ cm}$. Find the value of unknown resistance.

Solution :- $Q = 10 \Omega$; $l_1 = 55 \text{ cm}$; $l_2 = 100 - l_1 = 45 \text{ cm}$; $P = ?$

- From the theory of meter bridge ; $\frac{P}{Q} = \frac{l_1}{l_2}$
- (or) $P = Q \frac{l_1}{l_2} = 10 \times \frac{55}{45} = \frac{550}{45}$
- $P = 12.22 \Omega$

27. Find the heat energy produced in a resistance of 10Ω when 5 A current flows through it for 5 minutes .

Solution :- $R = 10 \Omega$; $I = 5 \text{ A}$; $t = 5 \text{ min} = 300 \text{ s}$; $H = ?$

- From Joule's law of heating,
- $$H = I^2 R t = 5^2 \times 10 \times 300 = 25 \times 3000$$
- $$H = 75000 \text{ J} = 75 \text{ kJ}$$

28. An electric heater of resistance 10Ω connected to 220 V power supply is immersed in the water of 1 kg . How long the electrical heater has to be switched on to increase its temperature from 30°C to 60°C . (Specific heat capacity of water is $s = 4200 \text{ J kg}^{-1} \text{ K}^{-1}$)

Solution :- $R = 10 \Omega$; $V = 220 \text{ V}$; $m = 1 \text{ kg}$; $T_1 = 30^\circ\text{C}$; $T_2 = 60^\circ\text{C}$; $t = ?$

- From Joule's law of heating ; $H = I^2 R t = \frac{V^2}{R} t$
- Heat absorbed by the water ; $H = m s \Delta T = m s (T_2 - T_1)$
- Here, heat produced by the heater in time 't' is equal to the heat absorbed by the water to increase its temperature (i.e.)

$$\frac{V^2}{R} t = m s (T_2 - T_1)$$

$$t = \frac{R}{V^2} m s (T_2 - T_1)$$

$$t = \frac{10}{220^2} \times 1 \times 4200 \times (60 - 30)$$

$$t = \frac{10}{220 \times 220} \times 4200 \times 30$$


$$t = \frac{4200 \times 3}{22 \times 22} = \frac{12600}{484} = 2.604 \times 10^1$$

$$t = 26.04 \text{ s}$$

No	Log
12600	4.1004
484	2.6848
(-)	1.4156
ALog	2.604×10^1

EXERCISE PROBLEMS

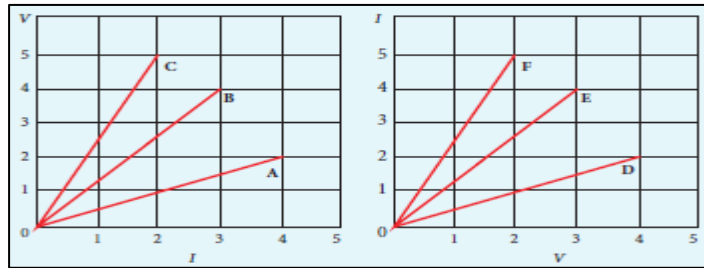1. The following graphs represent the current versus voltage and voltage versus current for the six conductors A,B,C,D,E and F. Which conductor has least resistance and which has maximum resistance?



Solution :-

Figure (1) :

- Resistance of conductor - A ; $R_A = \frac{\Delta V}{\Delta I} = \frac{2}{4} = 0.5 \Omega$
- Resistance of conductor - B ; $R_B = \frac{\Delta V}{\Delta I} = \frac{4}{3} = 1.33 \Omega$
- Resistance of conductor - C ; $R_C = \frac{\Delta V}{\Delta I} = \frac{5}{2} = 2.5 \Omega$

Figure (2) :

- Resistance of conductor - D ; $R_D = \frac{\Delta V}{\Delta I} = \frac{4}{2} = 2 \Omega$
- Resistance of conductor - E ; $R_E = \frac{\Delta V}{\Delta I} = \frac{3}{4} = 0.75 \Omega$
- Resistance of conductor - F ; $R_F = \frac{\Delta V}{\Delta I} = \frac{2}{5} = 0.4 \Omega$
- Thus conductor F has least resistance (i.e.) $R_F = 0.4 \Omega$
And conductor C has maximum resistance (i.e.) $R_C = 2.5 \Omega$

2. Lightning is very good example of natural current. In typical lightning, there is 10^9 J energy transfer across the potential difference of 5×10^7 V during a time interval of 0.2 s. Using this information, estimate the following quantities



(a) total amount of charge transferred between cloud and ground (b) the current in the lightning bolt (c) the power delivered in 0.2 s.

Solution :- $V = 5 \times 10^7$ V ; $t = 0.2$ s ; $U = 10^9$ J

(a) Total charge ; $Q = \frac{U}{V} = \frac{10^9}{5 \times 10^7} = \frac{1}{5} \times 10^2 = 0.2 \times 10^2 = 20$ C

(b) Current ; $I = \frac{Q}{t} = \frac{20}{0.2} = \frac{200}{2} = 100$ A

(c) Power ; $P = \frac{U}{t} = \frac{10^9}{0.2} = 5 \times 10^9$ W = 5 GW

3. A copper wire of 10^{-6} m² area of cross section, carries a current of 2 A. If the number of free electrons per cubic meter in the wire is 8×10^{28} , calculate the current density and average drift velocity of electrons.

Solution :- $A = 10^{-6}$ m² ; $I = 2$ A ; $n = 8 \times 10^{28}$; $J = ?$; $v_d = ?$

- Current density ;

$$J = \frac{I}{A} = \frac{2}{10^{-6}} = 2 \times 10^6 \text{ A m}^{-2}$$

- Average drift velocity ;

$$v_d = \frac{I}{n A e} = \frac{J}{n e}$$

$$v_d = \frac{2 \times 10^6}{8 \times 10^{28} \times 1.6 \times 10^{-19}} = \frac{1}{6.4} \times 10^{-3}$$

$$v_d = 1.562 \times 10^{-4} \text{ m s}^{-1} = 15.62 \times 10^{-5} \text{ m s}^{-1}$$

No	Log
1.	0.0000
6.4	0.8062
(-)	$\bar{1}.1938$
A/Log	1.562×10^{-1}

4. The resistance of a nichrome wire at 20°C is 10 Ω. If its temperature coefficient of resistivity of nichrome is 0.004/°C, find the resistance of the wire at boiling point of water. Comment on the result.

Solution :- $T_o = 0^\circ\text{C}$; $T = 100^\circ\text{C}$; $R_o = 10 \Omega$; $R_T = ?$

- Resistance of the conducting wire at T °C is,

$$R_T = R_o [1 + \alpha (T - T_o)]$$

$$R_T = 10 [1 + 0.004 (100 - 0)]$$


$$R_T = 10 [1 + 0.004 \times 100]$$

$$R_T = 10 [1 + 0.4] = 10 \times 1.4$$

$$R_T = 14 \Omega$$

- As the temperature increases the resistance of the wire also increases.

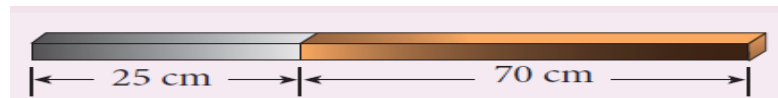5. The rod given in the figure is made up of two different materials. Both have square cross sections of 3 mm side. The resistivity of the first material is $4 \times 10^{-3} \Omega\text{m}$ and that of second material has resistivity of $5 \times 10^{-3} \Omega\text{m}$. What is the resistance of rod between its ends?



Solution :- $A = 3\text{mm} \times 3\text{mm} = 9 \text{mm}^2 = 9 \times 10^{-6} \text{m}^2$; $l_1 = 25 \text{cm} = 25 \times 10^{-2} \text{m}$
 $l_2 = 70 \text{cm} = 70 \times 10^{-2} \text{m}$; $\rho_1 = 4 \times 10^{-3}$; $\rho_2 = 5 \times 10^{-3}$

- Resistance of first material ;

$$R_1 = \frac{\rho_1 l_1}{A} = \frac{4 \times 10^{-3} \times 25 \times 10^{-2}}{9 \times 10^{-6}} = \frac{1000}{9} \Omega$$

- Resistance of second material ;


$$R_2 = \frac{\rho_2 l_2}{A} = \frac{5 \times 10^{-3} \times 70 \times 10^{-2}}{9 \times 10^{-6}} = \frac{3500}{9} \Omega$$

- Since the two materials are in series, their effective resistance,

$$R_{tot} = R_1 + R_2 = \frac{1000}{9} + \frac{3500}{9} = \frac{1000 + 3500}{9} = \frac{4500}{9}$$

$$R_{tot} = 500 \Omega$$

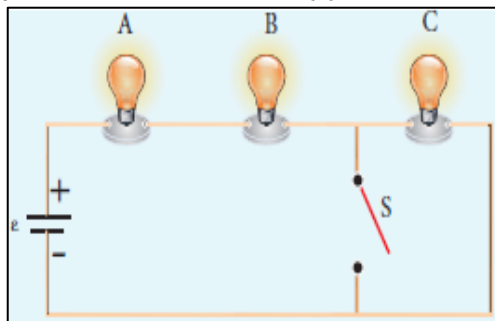6. Three identical lamps each having a resistance R are connected to the battery of emf ϵ as shown in the figure. Suddenly the switch S is closed. (a) Calculate the current in the circuit when S is open and closed (b) What happens to the intensities of the bulbs A, B and C. (c) Calculate the voltage across the three bulbs when S is open and closed (d) Calculate the power delivered to the circuit when S is opened and closed (e) Does the power delivered to the circuit decrease, increase or remain same?



Solution :-

(a) **Current :**

- When S is open, all the bulbs A, B and C are in series, and hence their effective resistance becomes ; $R_T = R + R + R = 3R$. Thus from Ohm's law,

$$I = \frac{\epsilon}{R_T} = \frac{\epsilon}{3R}$$

- When S is closed, only the bulbs A and B are in series and hence their effective resistance becomes $R_T = R + R = 2R$ and no current flows through bulb C. Thus from Ohm's law,

$$I = \frac{\epsilon}{R_T} = \frac{\epsilon}{2R}$$

(b) **Intensity :**

- When S is open, all the bulbs A, B and C are in series. Here current through all the bulbs are same. So all the bulbs glow with equal intensity.
- When S is closed, only the bulbs A and B are in series. The intensities of the bulbs A and B equally increase. Bulb C will not glow since no current pass through it.

(c) **Voltage (Potential difference) :**

- When S is open,

$$V_A = I R_A = \frac{\epsilon}{3R} \times R = \frac{\epsilon}{3}$$

$$V_B = I R_B = \frac{\epsilon}{3R} \times R = \frac{\epsilon}{3}$$

$$V_C = I R_C = \frac{\epsilon}{3R} \times R = \frac{\epsilon}{3}$$

- When S is closed,

$$V_A = I R_A = \frac{\epsilon}{2R} \times R = \frac{\epsilon}{2}$$

$$V_B = I R_B = \frac{\epsilon}{2R} \times R = \frac{\epsilon}{2}$$

$$V_C = 0$$

(d) **Power delivered :**

- When S is open,

$$P_A = V_A I = \frac{\epsilon}{3} \times \frac{\epsilon}{3R} = \frac{\epsilon^2}{9R}$$

$$P_B = V_B I = \frac{\epsilon}{3} \times \frac{\epsilon}{3R} = \frac{\epsilon^2}{9R}$$

$$P_C = V_C I = \frac{\epsilon}{3} \times \frac{\epsilon}{3R} = \frac{\epsilon^2}{9R}$$

$$\text{Total power delivered; } P_{tot} = P_A + P_B + P_C = 3 \left(\frac{\epsilon^2}{9R} \right) = \frac{\epsilon^2}{3R}$$

- When S is closed,

$$P_A = V_A I = \frac{\epsilon}{2} \times \frac{\epsilon}{2R} = \frac{\epsilon^2}{4R}$$

$$P_B = V_B I = \frac{\epsilon}{2} \times \frac{\epsilon}{2R} = \frac{\epsilon^2}{4R}$$

$$P_C = 0$$

$$\text{Total power delivered; } P_{tot} = P_A + P_B + P_C = 2 \left(\frac{\epsilon^2}{4R} \right) = \frac{\epsilon^2}{2R}$$

(e) When S is suddenly closed, the power delivered to the circuit will increase.

7. An electronics hobbyist is building a radio which requires 150Ω in her circuit. But she has only 220Ω , 79Ω and 92Ω resistors available. How can she connect the available resistors to get the desired value of resistance?

Solution :-


- The value of equivalent resistance in series connection will be greater than each individual resistance. Similarly the value of equivalent resistance in parallel connection will be lesser than each individual resistance.
- When all the three resistors are connected in series, their effective resistance will be greater than 220Ω and when all the three resistors are connected in parallel, their effective resistance will be less than 79Ω
- Initially first two resistors 220Ω and 79Ω are connected in parallel and their effective value,

$$\frac{1}{R_p} = \frac{1}{220} + \frac{1}{79} = \frac{220 + 79}{220 \times 79} = \frac{299}{17380}$$

$$\therefore R_p = \frac{17380}{299} = 5.811 \times 10^1 \Omega \approx 58 \Omega$$

No	Log
17380	4.2400
299	2.4757
(-)	1.7643
ALog	5.811×10^1

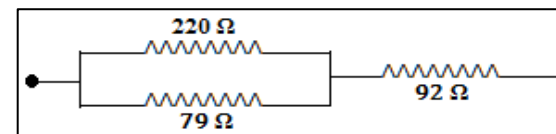- Now 58Ω and third resistor 92Ω are connected in series its effective value, $R_s = 58 + 92 = 150 \Omega$
- Thus in order to get 150Ω resistance, 220Ω and 79Ω are connected in parallel and this combination is connected in series with 92Ω



8. A cell supplies a current of 0.9 A through a 2 Ω resistor and a current of 0.3 A through a 7 Ω resistor. Calculate the internal resistance of the cell.


Solution :- $I_1 = 0.9 \text{ A}$; $I_2 = 0.3 \text{ A}$; $R_1 = 2 \Omega$; $R_2 = 7 \Omega$; $r = ?$

- From Ohm's law ($V = IR$),
 $\epsilon = I_1(R_1 + r) = 0.9(2 + r) \text{ ---- (1)}$
 $\epsilon = I_2(R_2 + r) = 0.3(7 + r) \text{ ---- (2)}$

- From equation (1) and (2)
 $0.9(2 + r) = 0.3(7 + r)$
 $1.8 + 0.9r = 2.1 + 0.3r$
 $0.9r - 0.3r = 2.1 - 1.8$
 $0.6r = 0.3$

$$r = \frac{0.3}{0.6} = \frac{1}{2} = 0.5 \Omega$$

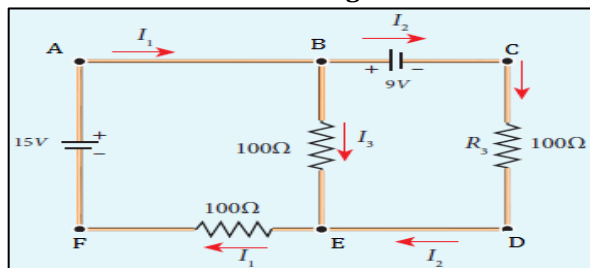9. Calculate the currents in the following circuit.



Solution :-

- Apply Kirchoff's current law at the junction B,
 $I_1 = I_2 + I_3 \text{ ---- (1)}$
- Apply Kirchoff's voltage law to the closed loop ABEFA and BCDEB,
 $100 I_3 + 100 I_1 = 15 \text{ ---- (2)}$
 and $100 I_2 - 100 I_3 = -9 \text{ ---- (3)}$

- Put equation (1) in (2)
 $100 I_3 + 100(I_2 + I_3) = 15$
 $100 I_3 + 100 I_2 + 100 I_3 = 15$
 $100 I_2 + 200 I_3 = 15 \text{ ---- (4)}$
 $(4) - (3) \Rightarrow 300 I_3 = 24$
 $I_3 = \frac{24}{300} = \frac{8}{100} = 0.08 \text{ A}$

- Put this in equation (3)
 $100 I_2 - 100(0.08) = -9$
 $100 I_2 - 8 = -9$
 $100 I_2 = -9 + 8 = -1$
 $I_2 = -\frac{1}{100} = -0.01 \text{ A}$


- Then equation(1) becomes,
 $I_1 = -0.01 + 0.08 = 0.07 \text{ A}$

- Thus, $I_1 = 0.07 \text{ A}$; $I_2 = -0.01 \text{ A}$; $I_3 = 0.08 \text{ A}$

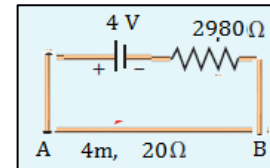10. A potentiometer wire has a length of 4 m and resistance of 20 Ω. It is connected in series with resistance of 2980 Ω and a cell of emf 4 V. Calculate the potential gradient along the wire.

Solution :- $l = 4 \text{ m}$; $R = 20 \Omega$; $R_{ex} = 2980 \Omega$; $\epsilon = 4 \text{ V}$; $V = ?$
 Resistance per unit length of the potentiometer wire, $r = \frac{20}{4} = 5 \Omega \text{ m}^{-1}$

- From Ohm's law ; $I = \frac{\epsilon}{(R + R_{ex})} = \frac{4}{(20 + 2980)} = \frac{4}{3000}$
 $I = \frac{4}{3 \times 10^3} = 1.33 \times 10^{-3} \text{ A}$



- Potential difference across the potentiometer wire
 $V = IR = 1.33 \times 10^{-3} \times 20 = 26.6 \times 10^{-3} \text{ V}$
- Then the potential gradient along the wire
 $V = Ir = 1.33 \times 10^{-3} \times 5 = 6.65 \times 10^{-3} \text{ Vm}^{-1}$

11. Determine the current flowing through the galvanometer (G) as shown in the figure.

Solution :-

- Apply Kirchoff's current law at the junction P,
 $2 = I_1 + I_2 \text{ (or)}$
 $I_2 = 2 - I_1 \text{ ---- (1)}$
- Apply Kirchoff's voltage law to the closed loop PQSP,

$$5 I_1 + 10 I_g - 15 I_2 = 0$$

$$5 I_1 + 10 I_g - 15(2 - I_1) = 0$$

$$5 I_1 + 10 I_g - 30 + 15 I_1 = 0$$

$$20 I_1 + 10 I_g - 30 = 0$$

$$20 I_1 + 10 I_g = 30 \text{ ---- (2)}$$

- Similarly Apply Kirchoff's voltage law to the closed loop QRSQ,

$$10(I_1 - I_g) - 10 I_g - 20(I_2 + I_g) = 0$$

$$10 I_1 - 10 I_g - 10 I_g - 20 I_2 - 20 I_g = 0$$

$$10 I_1 - 40 I_g - 20 I_2 = 0$$

$$10 I_1 - 40 I_g - 20(2 - I_1) = 0$$

$$10 I_1 - 40 I_g - 40 + 20 I_1 = 0$$

$$30 I_1 - 40 I_g - 40 = 0$$

$$30 I_1 - 40 I_g = 40 \text{ ---- (3)}$$


$$(2) \times 3 \Rightarrow 60 I_1 + 30 I_g = 90 \text{ ---- (4)}$$

$$(3) \times 2 \Rightarrow 60 I_1 - 80 I_g = 80 \text{ ---- (5)}$$

$$(4) - (5) \Rightarrow 110 I_g = 10$$

$$11 I_g = 1$$


$$I_g = \frac{1}{11} \text{ A}$$

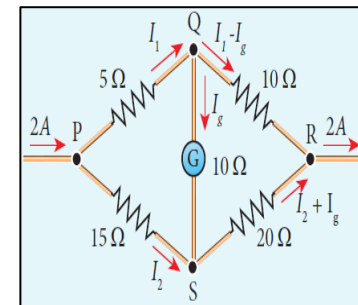

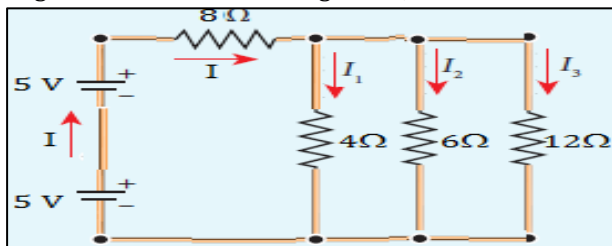12. Two cells each of 5V are connected in series with a 8 Ω resistor and three parallel resistors of 4 Ω, 6 Ω and 12 Ω. Draw a circuit diagram for the above arrangement. Calculate (i) the current drawn from the cells (ii) current through each resistor

Solution :-

- ◆ Circuit diagram for the above arrangement,



(i) **The current drawn from the cells :**

- ◆ Here, 4Ω, 6 Ω and 12 Ω all are in parallel, their effective resistance,

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{6} + \frac{1}{12} = \frac{3+2+1}{12} = \frac{6}{12} = \frac{1}{2} \quad (\text{or}) \quad R_p = 2 \Omega$$

- ◆ Also, 8 Ω and 2 Ω are in series, their effective resistance,

$$R_s = 8 + 2 = 10 \Omega$$

- ◆ Total potential difference(voltage) ; $V = 5 + 5 = 10 V$

- ◆ Then current in the circuit,

$$I = \frac{V}{R_s} = \frac{10}{10} = 1 A$$

- ◆ The potential difference across parallel combination of effective resistance $R_p = 2 \Omega$ is ; $V_p = I R_p = 1 \times 2 = 2 V$


(ii) **Current through each resistor :**

- Current through 8 Ω resistor ; $I = 1 A$
- Current through 4 Ω resistor ; $I_1 = \frac{V_p}{4} = \frac{2}{4} = 0.5 A$
- Current through 6 Ω resistor ; $I_2 = \frac{V_p}{6} = \frac{2}{6} = 0.33 A$
- Current through 12 Ω resistor ; $I_3 = \frac{V_p}{12} = \frac{2}{12} = 0.17 A$

13. Four bulbs P, Q, R, S are connected in a circuit of unknown arrangement. When each bulb is removed one at a time and replaced, the following behavior is observed. Draw the circuit diagram for these bulbs.

	P	Q	R	S
P removed	*	on	on	on
Q removed	on	*	on	off
R removed	off	off	*	off
S removed	on	off	on	*

Solution :-

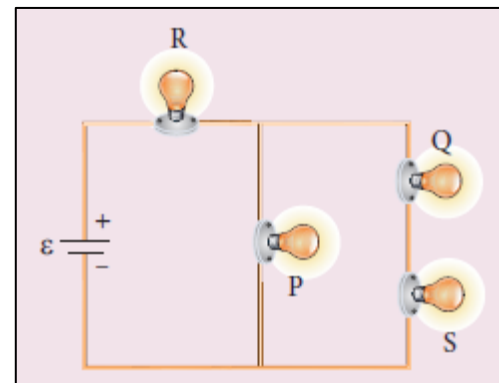

14. In a potentiometer arrangement, a cell of emf 1.25 V gives a balance point at 35 cm length of the wire. If the cell is replaced by another cell and the balance point shifts to 63 cm, what is the emf of the second cell?

Solution :- : $\epsilon_1 = 1.25 V$; $l_1 = 35 cm$; $l_2 = 63 cm$; $\epsilon_2 = ?$

- ◆ The ratio of emf's of two cells using potentiometer,

$$\frac{\epsilon_1}{\epsilon_2} = \frac{l_1}{l_2}$$

$$\epsilon_2 = \epsilon_1 \frac{l_2}{l_1}$$

$$\epsilon_2 = 1.25 \times \frac{63 \times 10^{-2}}{35 \times 10^{-2}} = \frac{78.75}{35}$$

$$\epsilon_2 = 2.25 V$$